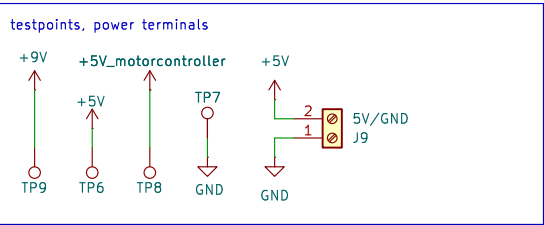
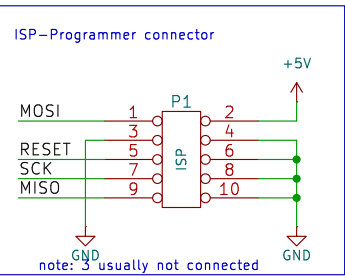
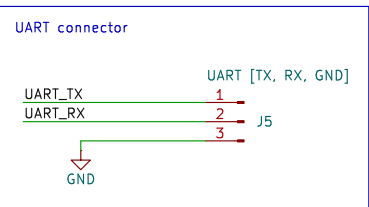
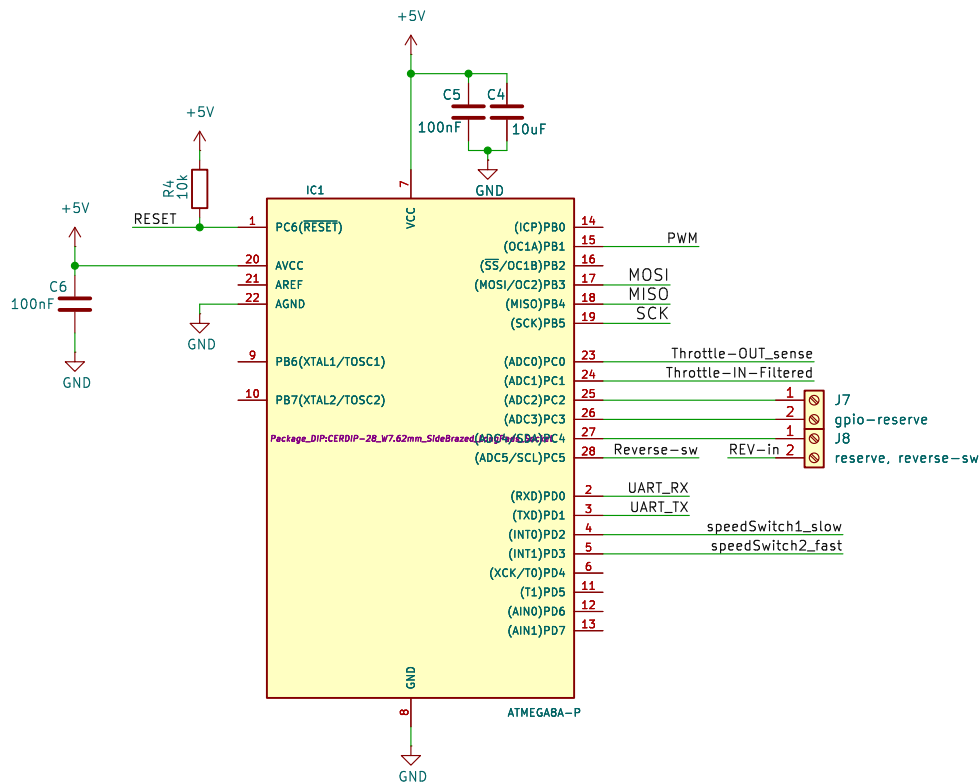
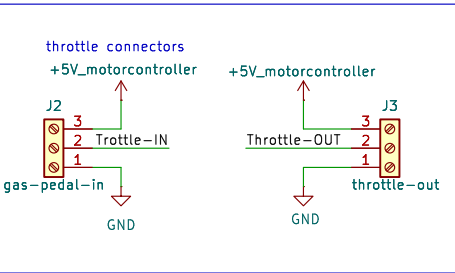
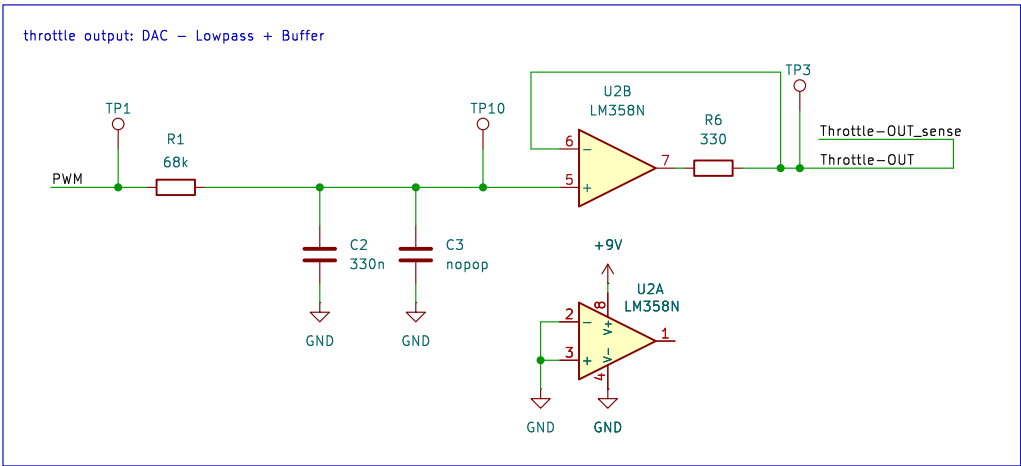
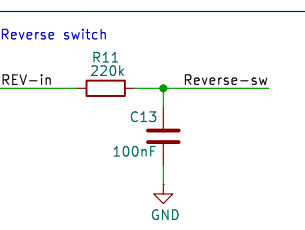
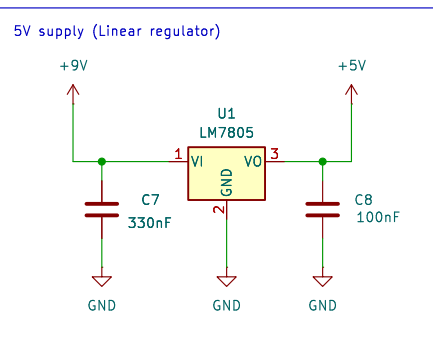
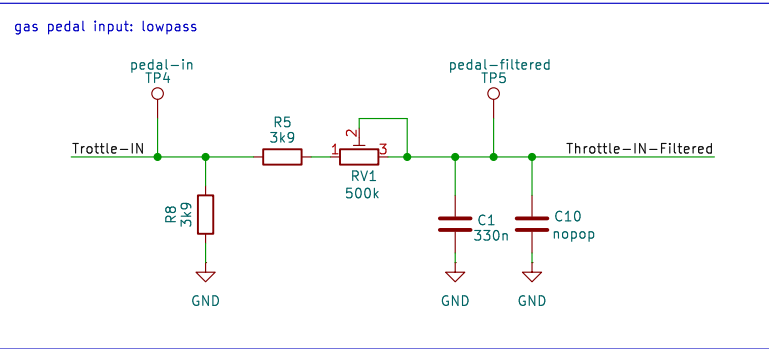
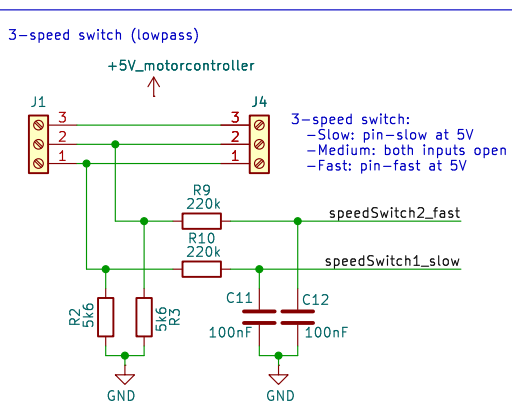


Note: additional 9V (>5V) supply necessary because
1. no rail-to-rail opamp available
2. motorcontroller does not provide sufficient 5V for this circuit
(there seems to be a series resistor when using throttle supply cable – drops to 4V)



Scale gas pedal voltage differently for 3000W BLDC motorcontroller